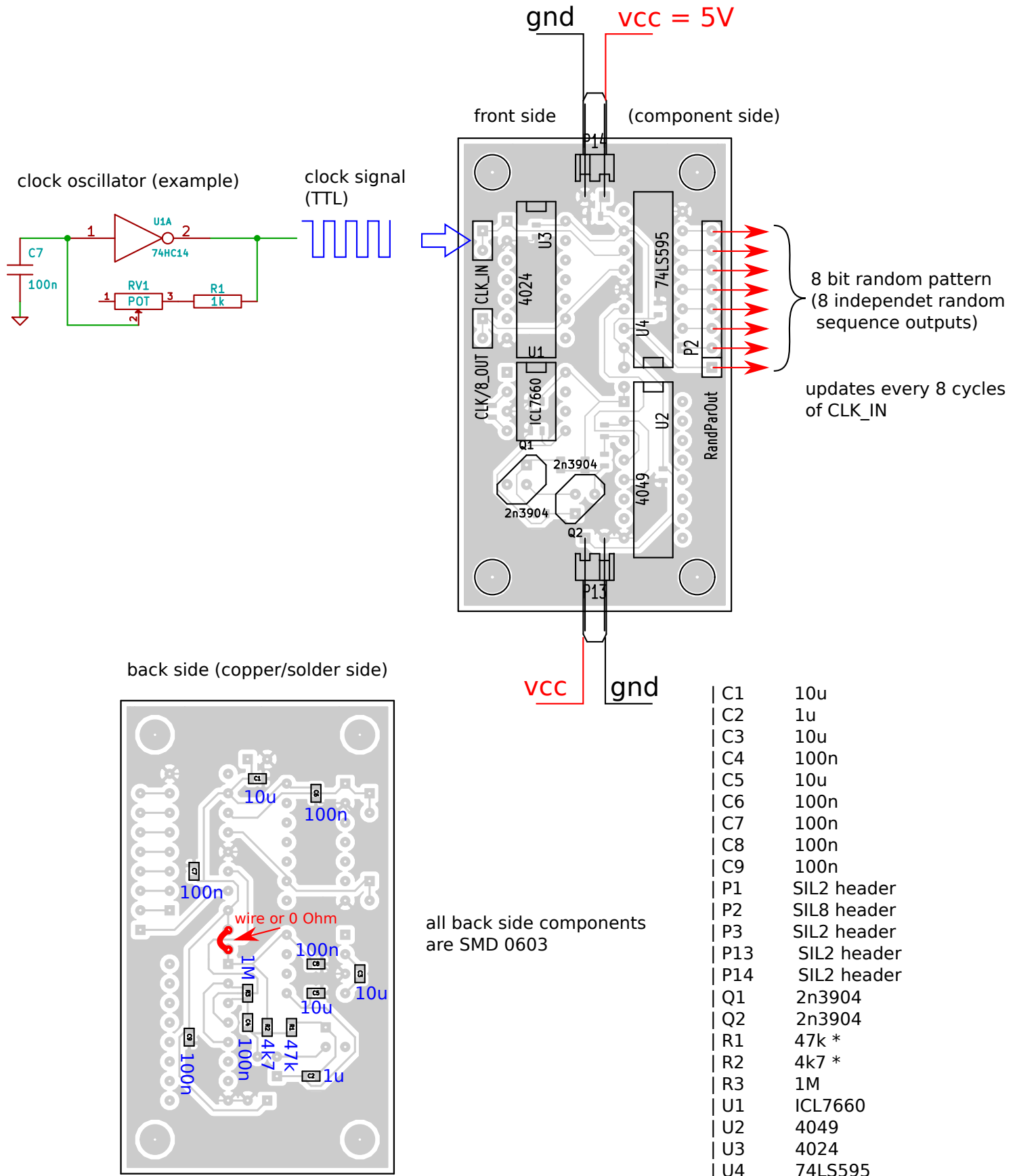


8 bit random pattern generator (e.g. for CMOS synthesizers) v0.1



* circuit also works with R1=100k, R2=10k